

Total No. of Pages 03

Third Semester

End Semester (Supplementary) Examination

Time: 3 Hours

Roll No.....

B. Tech(EL/EE)

Feb-2019

Maximum Marks: 40

EE/EL-203 ELECTRONIC DEVICES AND CIRCUITS

Note: Question 1 is compulsory.


Attempt Eight more Questions.

Assume suitable value for missing data (if any).

1 Fill up the blanks with suitable answers

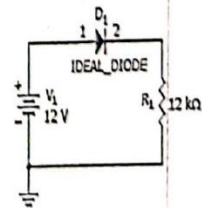
- (i) The input impedance of an ideal voltage amplifier should be
- (ii) Bandwidth of an ideal transresistance amplifier should be
- (iii) A voltage gain of 120 dB when expressed as a dimensionless quantity is equal to
- (iv) For a silicon pn-junction having reverse saturation current of 30 nA at 300 K with a V_T of 26 mV the forward bias required to produce a current of 0.1 mA and 10 mA respectively, will be..... and
- (v) In the forward active mode of operation of a BJT the collector-base junction is biased.
- (vi) The dynamic resistance r_d of a forward biased diode depends on.....
- (vii) The terminal voltage in a npn transistor were measured and found as $V_E = -2.7V$, $V_B = -2.0V$ and $V_C = 0V$. The transistor is operating inmode.

2[a] What is the current through the diode




108

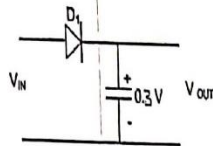- 2[b] Assuming $V_N = V_p \sin \omega t$ plot the output waveform of the circuit shown below for an initial capacitor voltage of 0.3V across the capacitor.



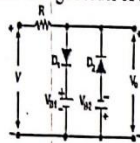
- 3 Plot the input/output characteristics of the circuit shown below assuming the constant voltage model of the diode.




- 4 A centre tap full wave rectifier has the load resistance $R_L = 1K\Omega$. The forward resistance R_F of each diode is 10Ω . The voltage across half of secondary winding is given by the equation $v = 200 \sin 314t$. Determine:

- The peak and average value of current
- The rms value of current
- The ripple factor
- The rectification efficiency

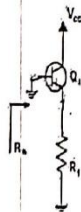- 5 Compute the input impedance of the circuit given below. Take V_A to be infinite.



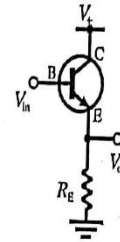- 6 Draw the small signal model of the circuit below and determine its voltage gain and output impedance.



- 7 Draw the circuit diagram of a common source amplifier along with the biasing diagram (fixed-bias) and derive expression for its voltage gain, input and output resistance

- 8 Draw the circuit diagram of a BJT differential amplifier loaded with passive resistors and biased with a constant current source. Using small signal model and the concept of half circuits determine the common mode gain, and differential mode input resistance.

- 9 For the following feedback configurations draw the schematic diagram and compute the input and output impedance:

- Voltage-current
- Current-current

- 10 Derive the expression to study the effect of C_s , C_c and C_E on the low frequency response of a common base npn transistor in a fixed biased configuration

- 11 Write short notes on any TWO of the following:

- Enhancement and Depletion type MOSFET
- Avalanche and Zener breakdown
- Properties of negative feedback

END